


Energy Storage

5. Introduction to Power Converters

Assoc. prof. Hrvoje Pandžić

Mateo Beus, MEE

Conversion of Electric Power

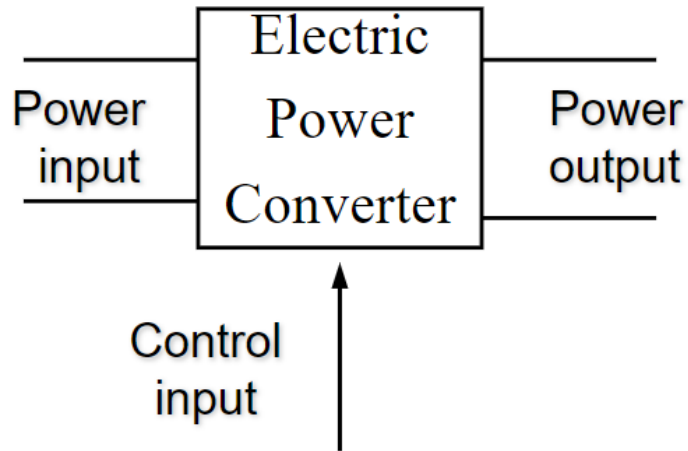

□ Other names for electric power converter:


- Power converter
- Converter
- Switching converter
- Power electronic circuit
- Power electronic converter

Two types of electric power	Changeable properties in conversion
DC(Direct Current)	Magnitude
AC (Alternating Current)	Frequency, magnitude, number of phases

Classification of Power Converters


Power input \ Power output		
	DC	AC
AC	AC to DC converter (Rectifier)	AC to AC converter (Fixed frequency : AC controller Variable frequency: Cycloconverter or frequency converter)
DC	DC to DC converter (Chopper)	DC to AC converter (Inverter)

Power Converter

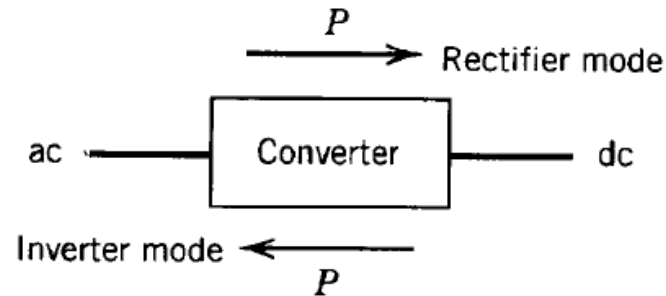


- ❑ Converter is a general term – an AC/DC converter is shown above.
 - Rectifier Mode of operation when power from AC to DC
 - Inverter Mode of operation when power from DC to AC
- ❑ Power converters can also convert
 - DC-to-DC
 - AC-to-AC
- ❑ Practical switching devices are selected based on their power handling rating – the product of their voltage and current rating – rather than their power dissipation ratings.


Elements of Power Electronic Devices

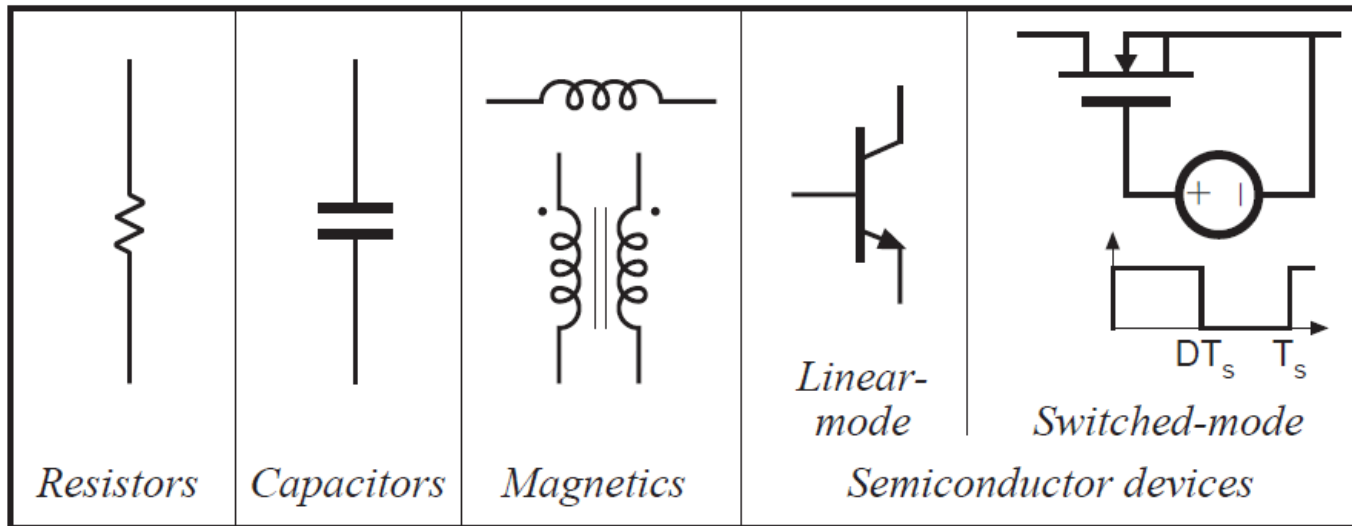

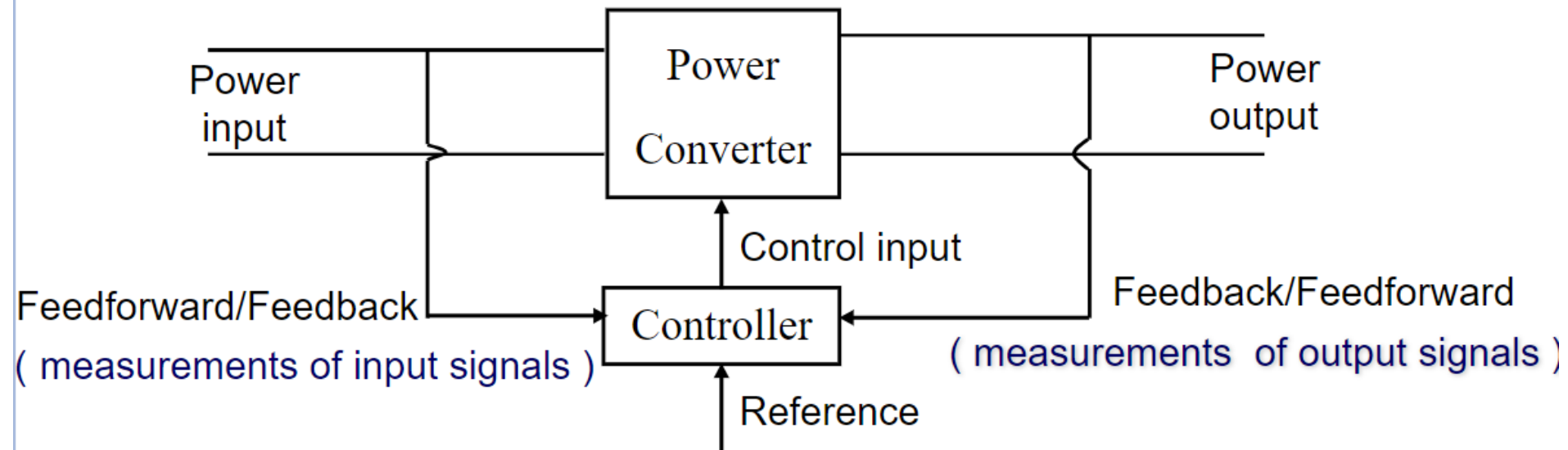
Generic Structure of a Power Electronic System



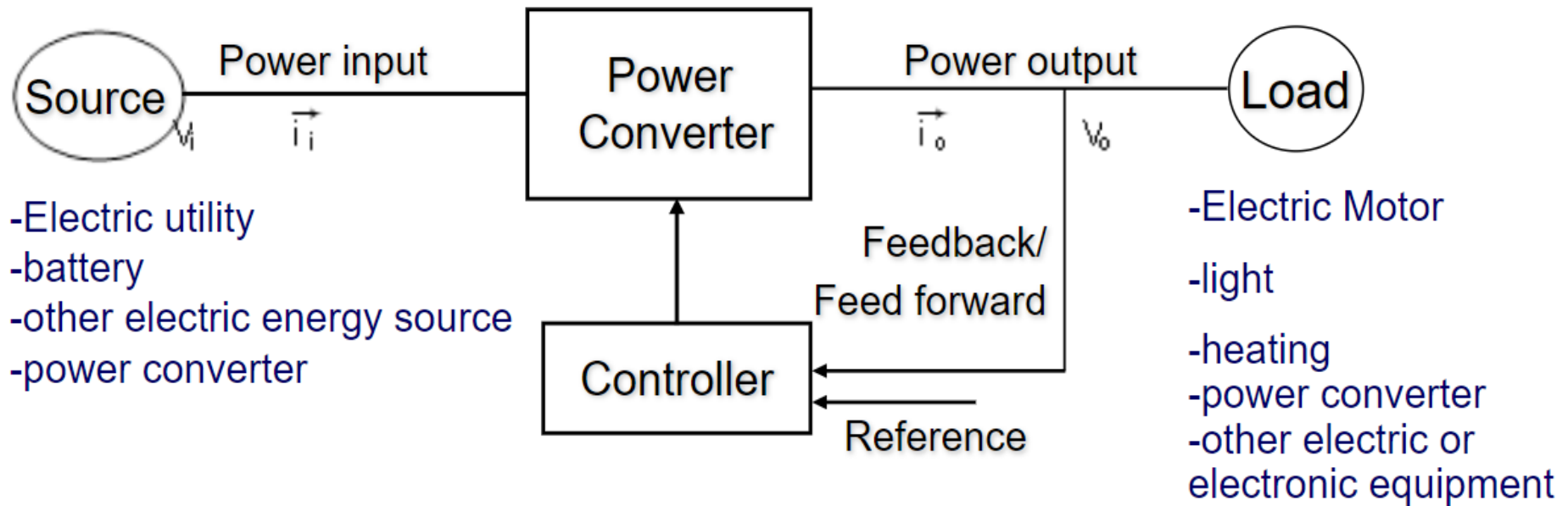Typical Power Sources and Loads for Power Electronic System



Relation with Other Disciplines

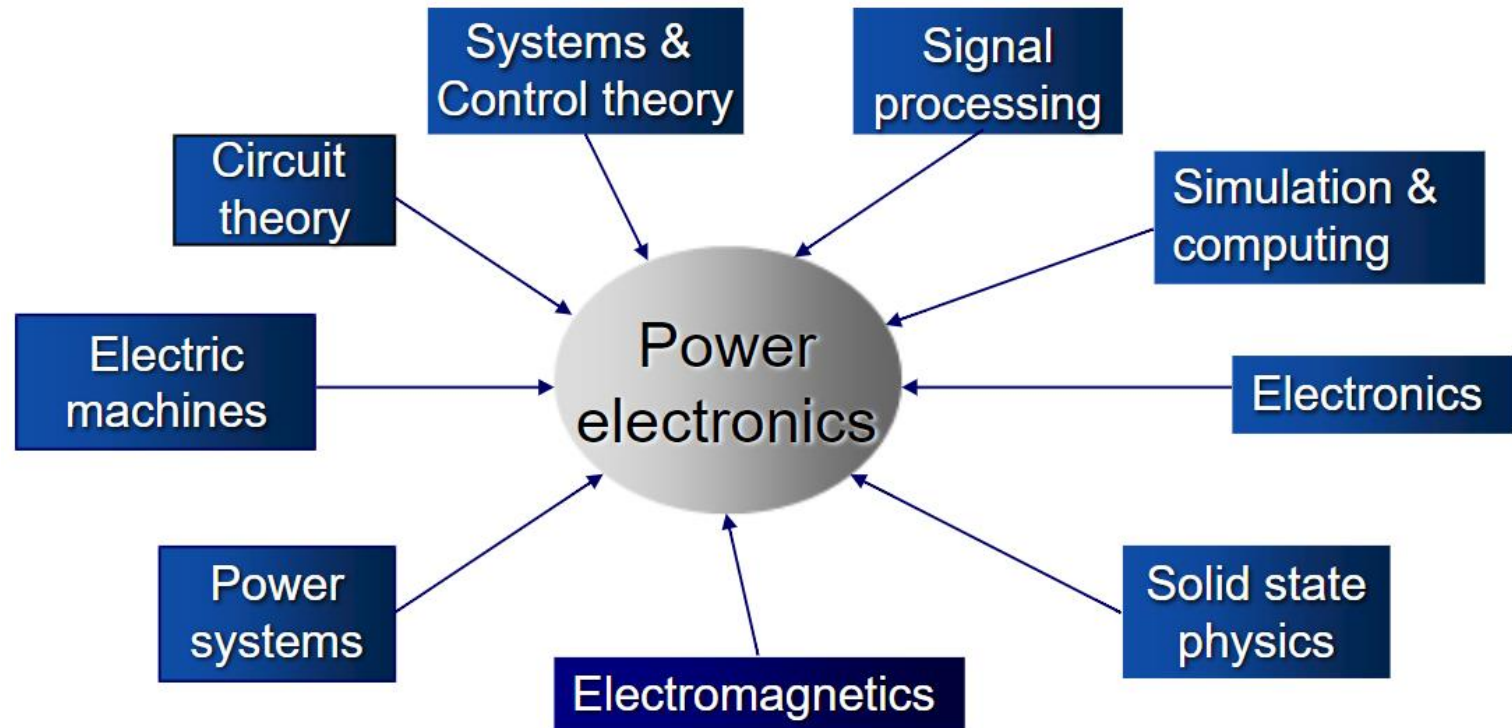

Power electronics is currently the most active discipline in electric power engineering worldwide.

Power Electronic Applications

Residential

- Refrigeration and freezers
- Heating
- Air conditioning
- Cooking
- Lightning

Commercial

- Heating, ventilating, and air conditioning
- Central refrigeration
- Lightning
- Computers and office equipment
- Uninterruptible power supplies (UPSs)
- Elevators

Industrial

- Pumps
- Compressors
- Welding
- Induction heating

Transportation

- Traction control of electric vehicles
- Battery chargers for electric vehicles
- Electric locomotives
- Street cars, trolley buses
- Subways

Utility systems

- High-voltage dc transmission (HVDC)
- Static var compensation (SVC)
- Renewable energy resources (wind, PV)
- Energy storage systems

Aerospace

- Aircraft power systems
- Satellite power systems

Telecommunications

- Battery chargers
- Power supplies (DC and UPS)

Power Electronics Applications – AC Motor Drive


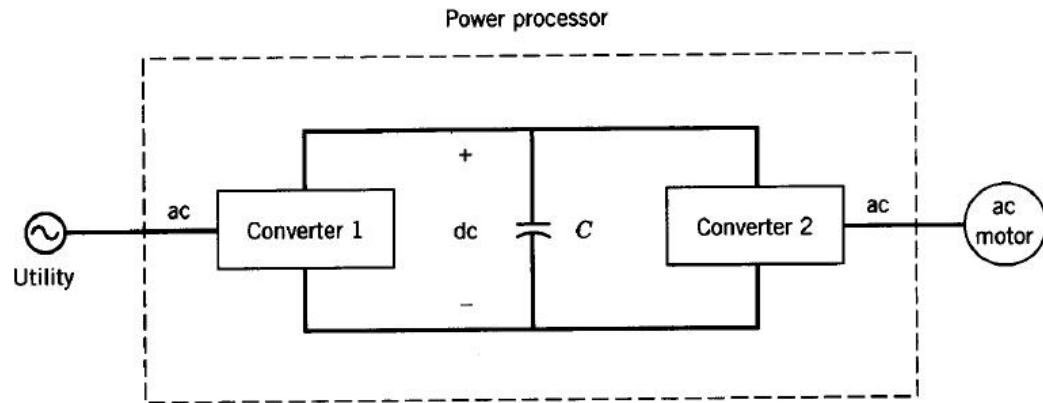


Figure 1-8 Block diagram of an ac motor drive.

- ❑ Converter 1 rectifies line-frequency AC into DC
- ❑ Capacitor acts as a filter – stores energy and decouples the two converters
- ❑ Converter 2 inverts DC to variable frequency AC – as needed by the motor.

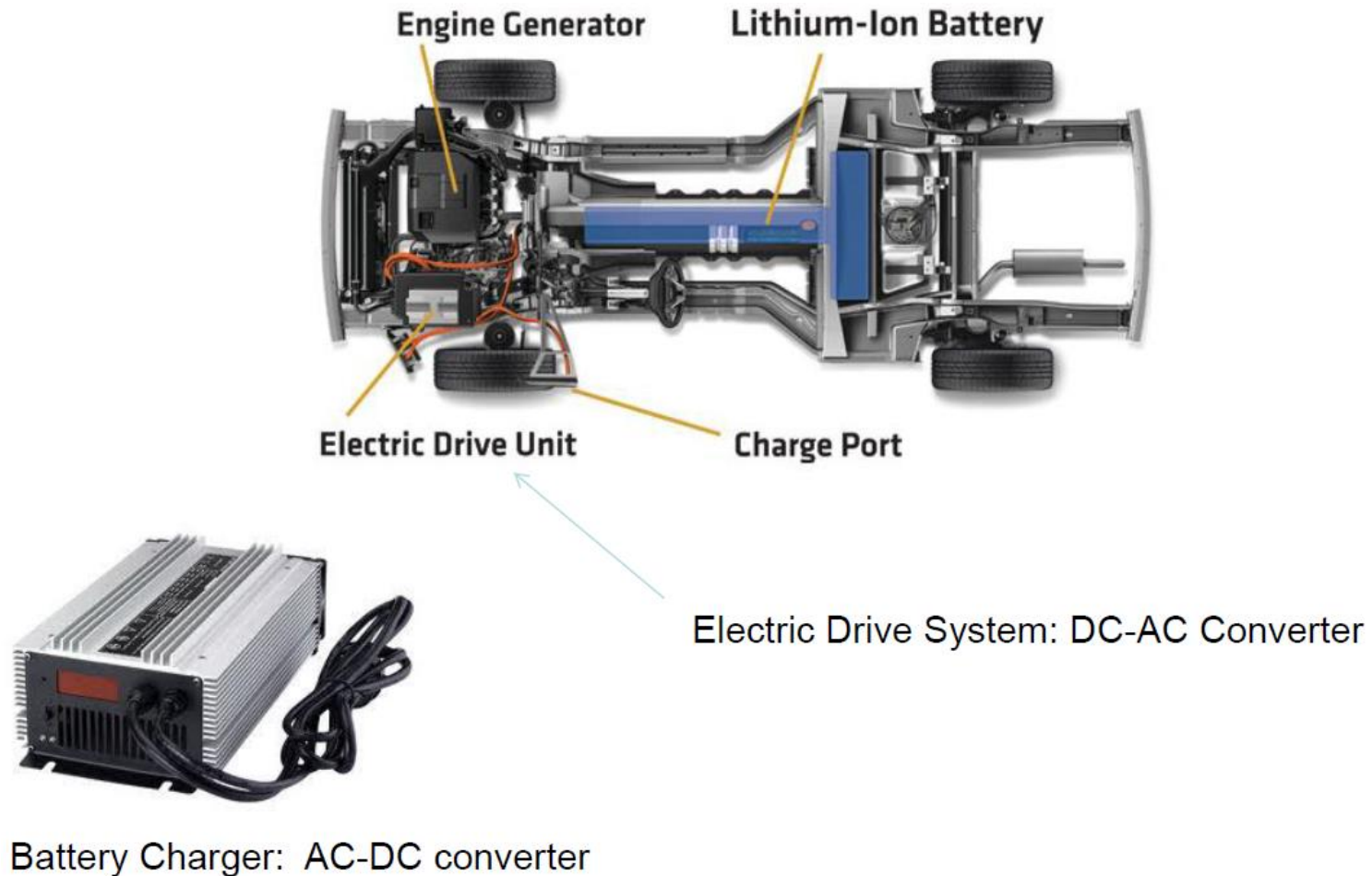Power Electronics Applications – Pure Electric and Plug-In Hybrid Vehicles




Power Electronics Applications – Renewable Energy Resources (PV)



PV Inverter: DC-AC Converter

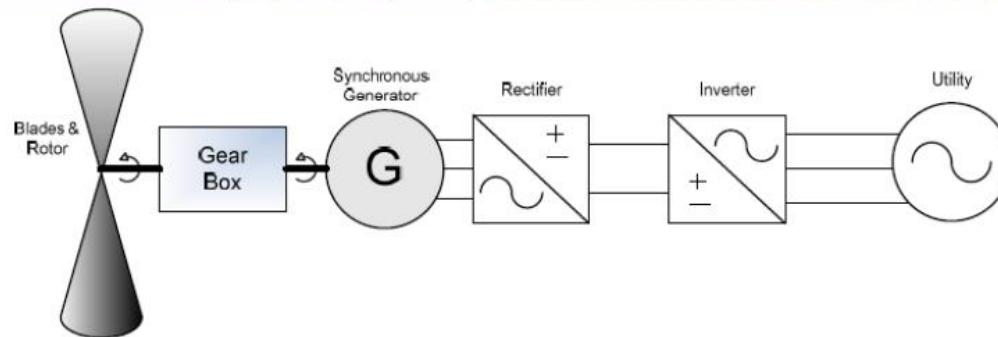Power Electronic Applications – Renewable Energy Resources (Wind)



The rectifier-inverter converts variable-frequency AC to fixed line-frequency AC.

Nonisolated/isolated Power Electronics Converters

- Non-isolated power electronic converters – the circuit does not consist of magnetic or electric insulation
- Isolated power electronic converters – the circuit consists of magnetic or electric insulation

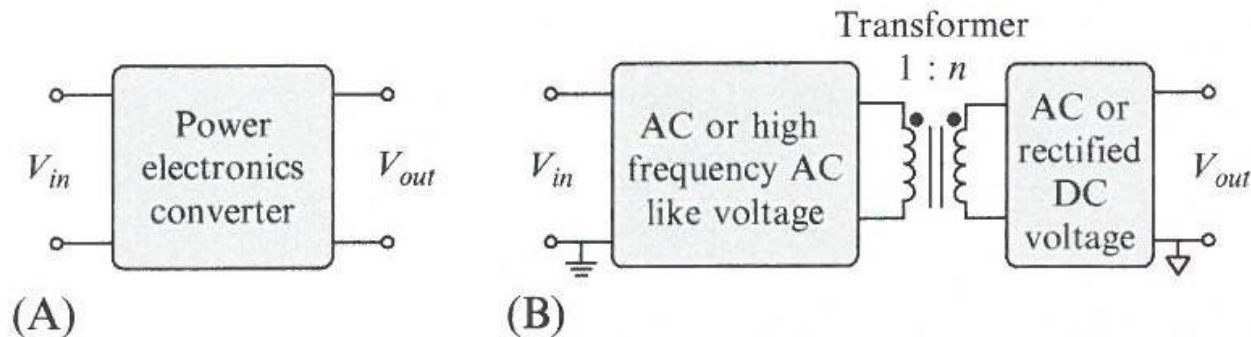


FIG. 1.1 General layouts of (A) nonisolated and (B) isolated power electronics converters.

Voltage-Fed/Current-Fed

- Depending on input circuitry power electronics converters can be classified as either voltage-or current-fed converters

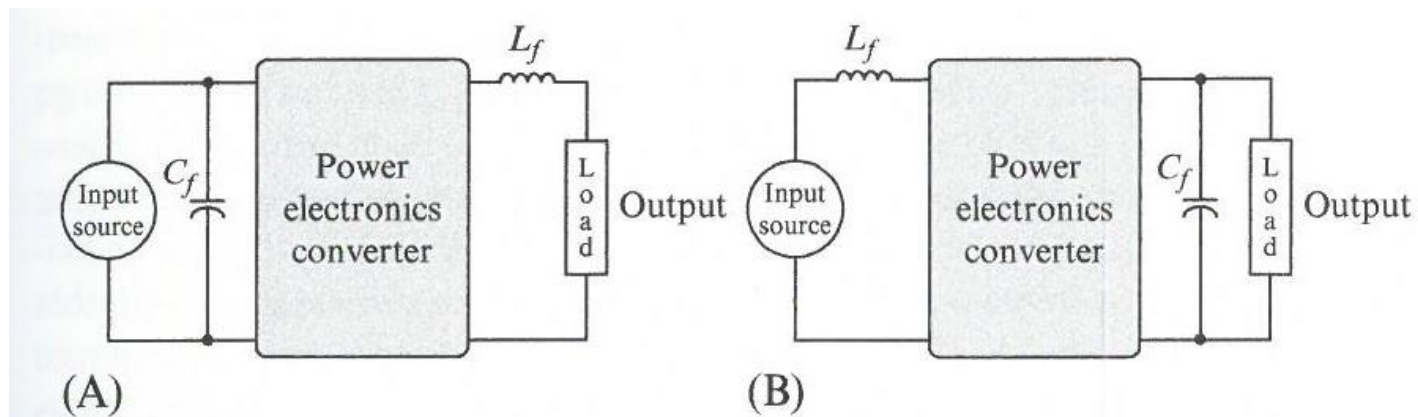


FIG. 1.2 General layout of (A) voltage-fed and (B) current-fed power electronics converters.

AC-to-DC Converter Topologies – Single-phase Half/full Wave Rectifier

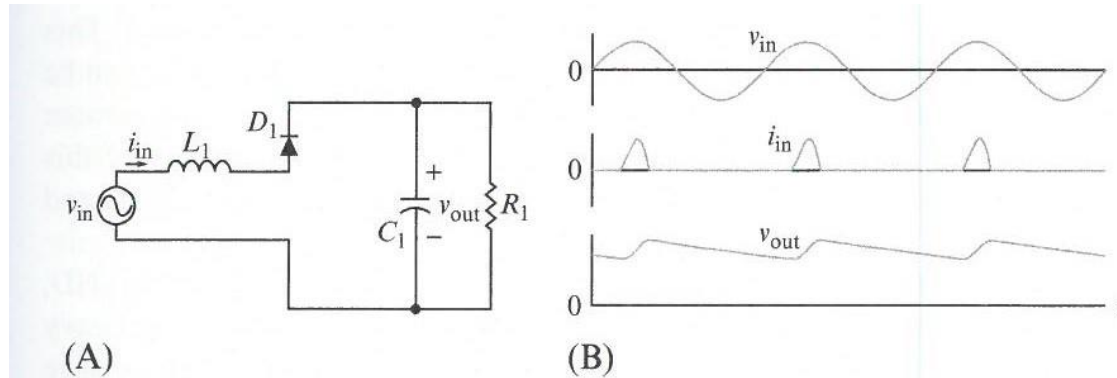


FIG. 1.4 Half-wave rectifier: (A) circuit diagram and (B) its waveforms.


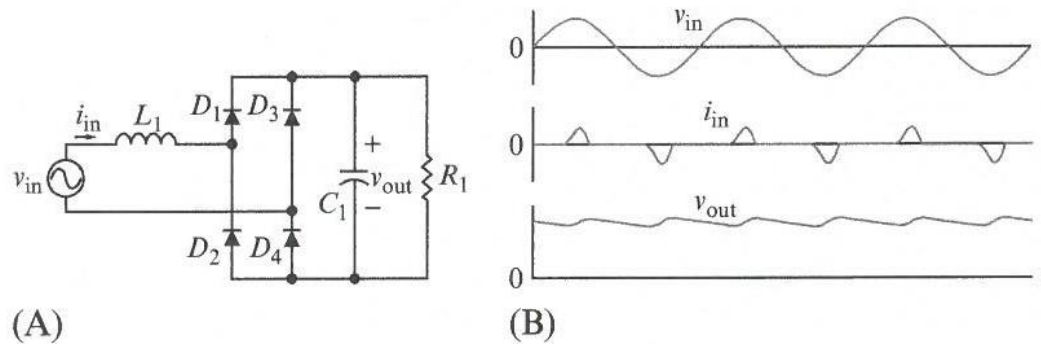


FIG. 1.5 Full-wave rectifier: (A) circuit diagram and (B) its waveforms.

AC-to-DC Converter Topologies


- ❑ An AC-to-DC converter converts AC voltage to a stable DC output voltage.
- ❑ Unidirectional AC to DC converters are also called rectifiers. The simplest construction of a rectifier is made from diodes.
- ❑ Diode rectifiers create nonnegligible distortion in its current and thus require a significant effort in filter design so that the distortion does not affect the AC grid.
- ❑ Half-wave rectifier converts single-phase AC voltage to DC voltage via single diode.
- ❑ Full-wave rectifier employs four diodes to convert both positive and negative cycles to the DC side before stabilizing the output voltage with the capacitor.

Example – Half-wave Rectifier

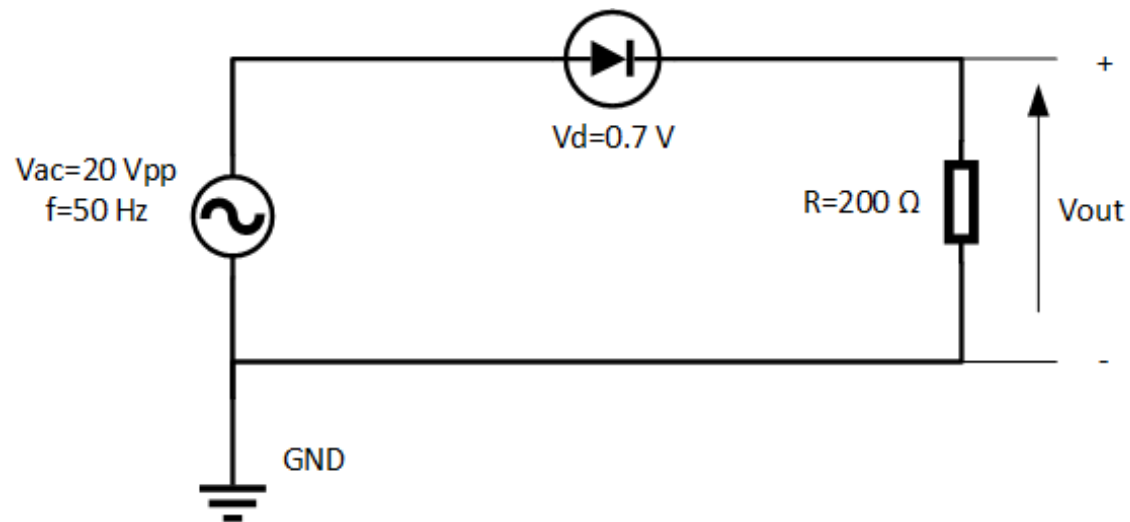

Output Voltage as a Function of Time - solution

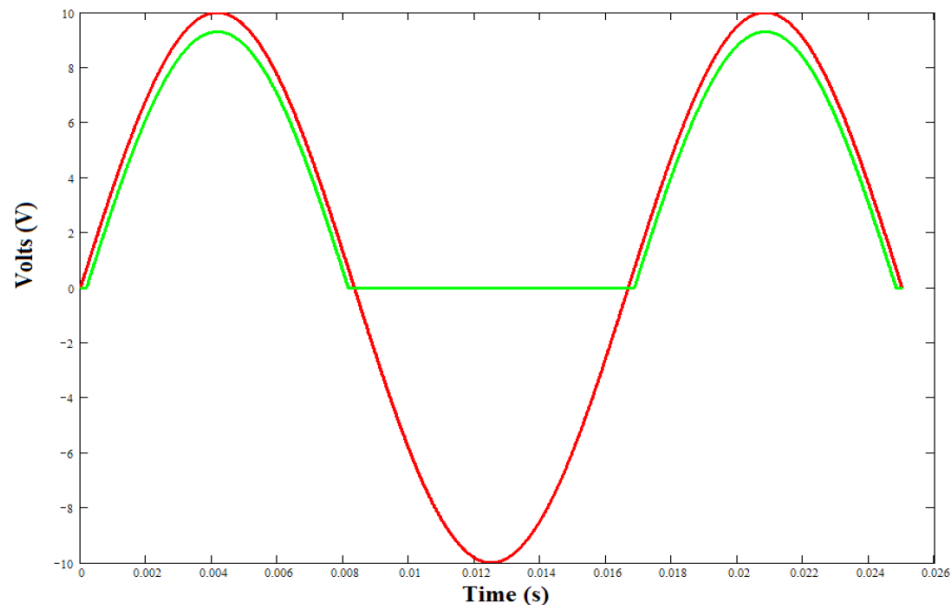- Since the input voltage was actually an AC power supply, the output voltage must vary with time.
 - The maximum output voltage is 9.3 V.
 - The output voltage is 0V when input voltage is 0.7 V.
 - The minimum output voltage is 0V.



AC-to-DC Converter Topology – Three-phase Rectifier

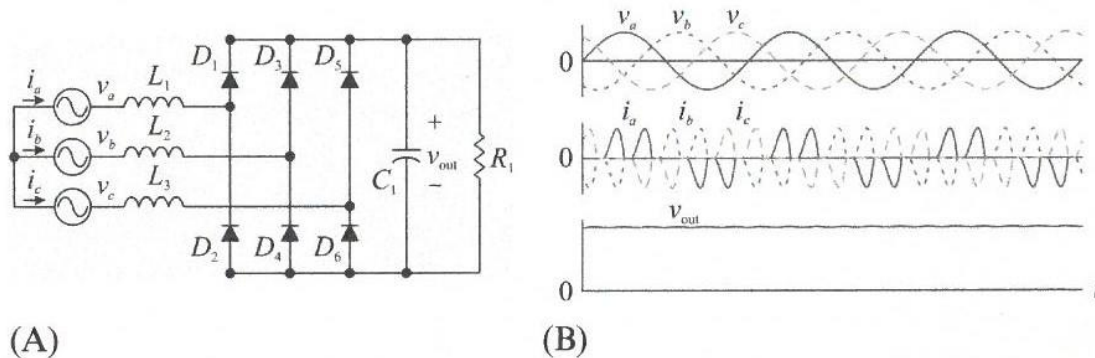


FIG. 1.6 Three-phase rectifier: (A) circuit diagram and (B) its waveforms.

DC-to-AC Converter Topologies

- DC-to-AC converters or an inverter is a device that produce an AC output of a definite phase, frequency and magnitude from a DC source.
- Based on the type of the source and load inverters are segregated into two distinct categories: voltage source inverters (VSIs) and Current Source Inverters (CSI).

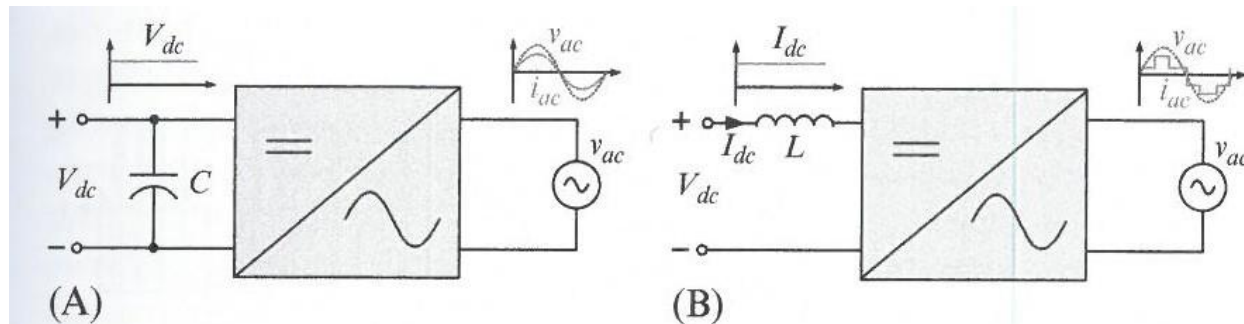


FIG. 1.16 DC-AC converter topologies: (A) VSI topology and (B) CSI topology.

Single-Phase DC-to-AC Converter

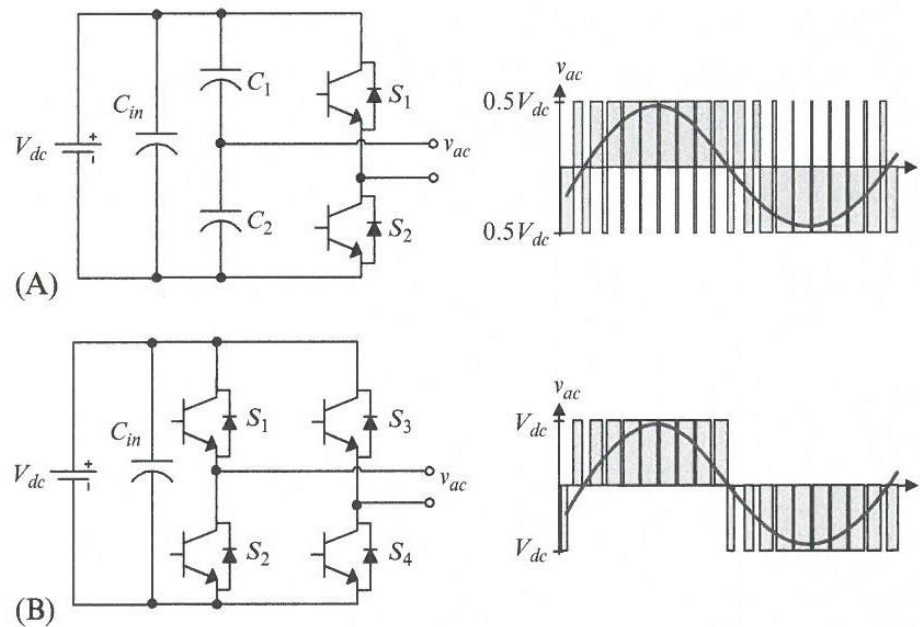


FIG. 1.18 Voltage source inverter showing its AC output voltage for the SPWM: (A) half-bridge and (B) full-bridge.

Three-Phase DC-to-AC Converter

□ DC-AC

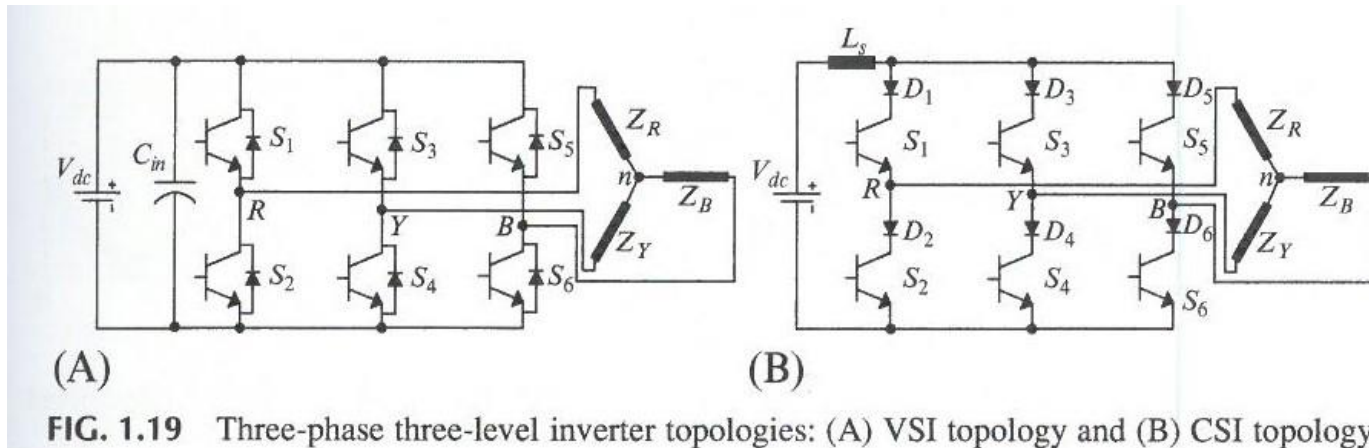


FIG. 1.19 Three-phase three-level inverter topologies: (A) VSI topology and (B) CSI topology.

DC-to-DC Converters

- ❑ A DC-DC converter changes the DC input to a higher or lower DC output voltage.
- ❑ The DC equivalent of an AC transformer.

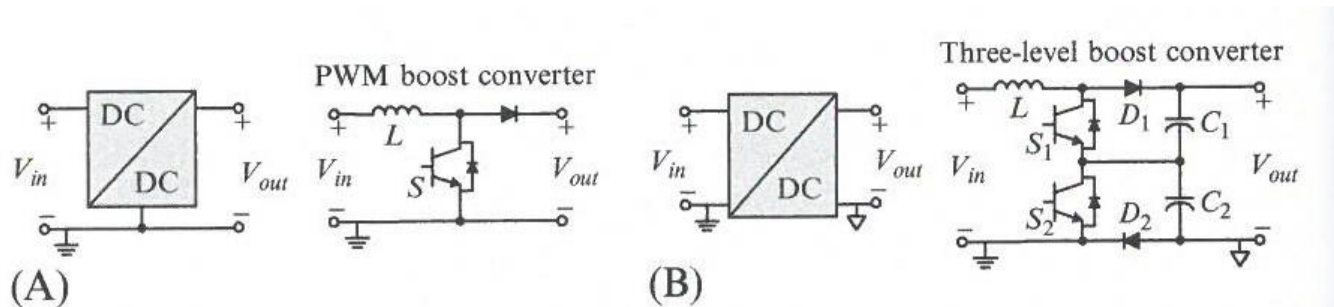


FIG. 1.24 Nonisolated DC-DC converters, (A) common grounded nonisolated DC-DC converter and (B) floated output nonisolated DC-DC converter.

Buck Converters

- A DC-DC converter changes the DC input to a lower DC output voltage.

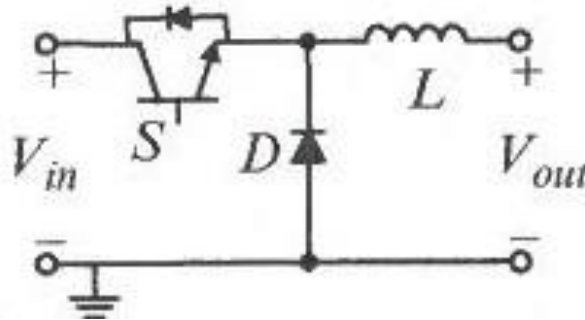


FIG. 1.25 Nonisolated DC-DC converters: Buck converter

Boost Converters

- A DC-DC converter changes the DC input to a higher DC output voltage.

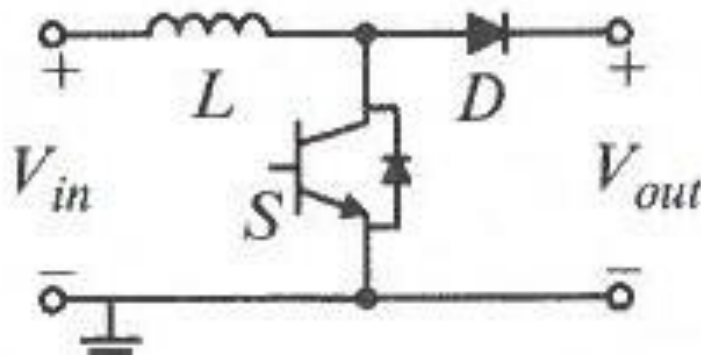


FIG. 1.26 Nonisolated DC-DC converters: Boost converter

Buck-Boost Converters

- A buck-boost converter can simultaneously step-down and step-up the input voltage.


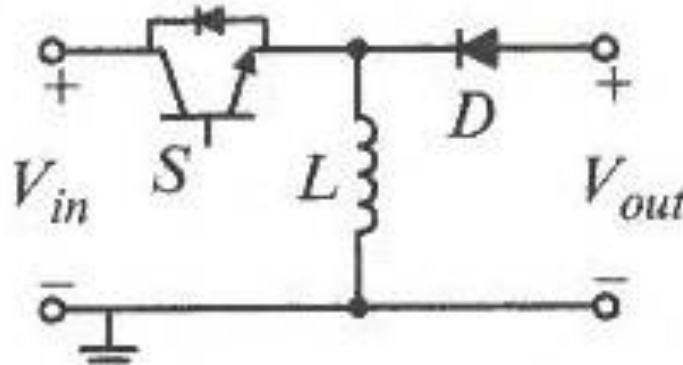


FIG. 1.26 Nonisolated DC-DC converters: Buck-Boost converter

Switching Function (switch control)

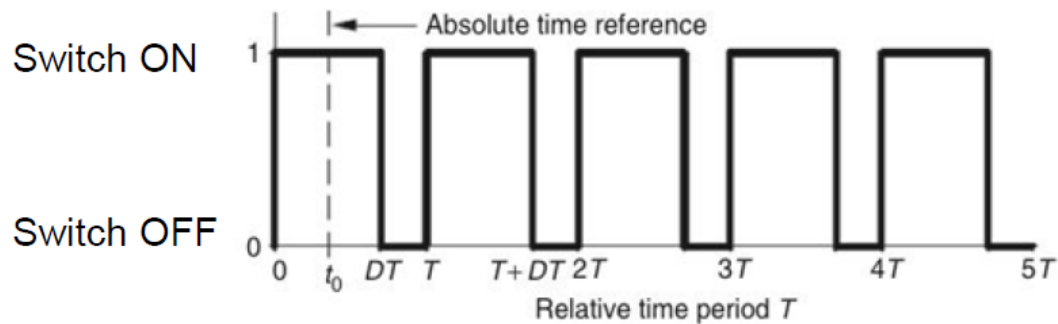

- T : period
- t_0 : time delay
- $f=1/T$: switching frequency
- D : duty ratio – fraction of time during which the switch is ON

AC-to-AC Converters

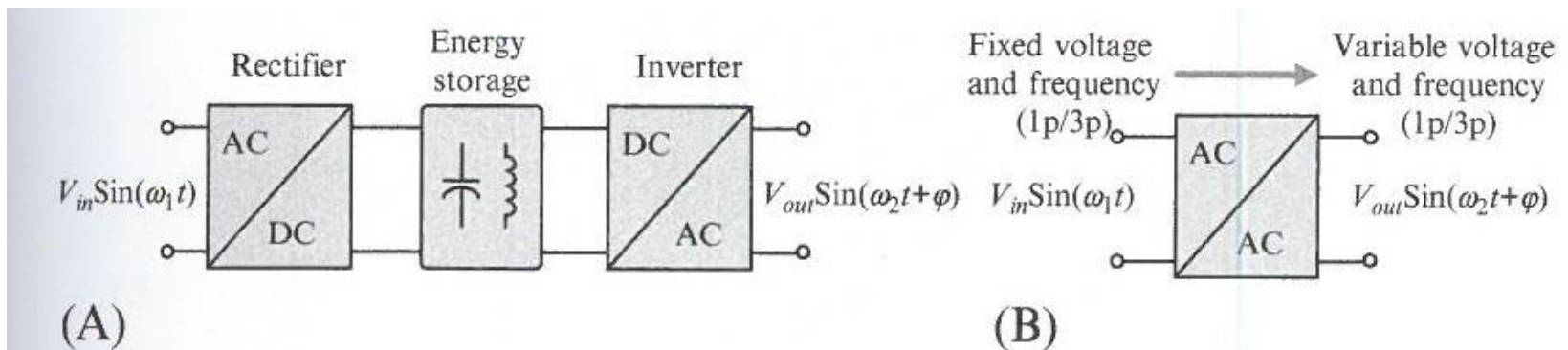


FIG. 1.28 General layouts of AC-AC converters, (A) indirect AC-AC converter and (B) direct AC-AC converter.

References

- Frede Blaabjerg, “Control of Power Electronic Converters and Systems”, Volume I, Academic Press 2018.